
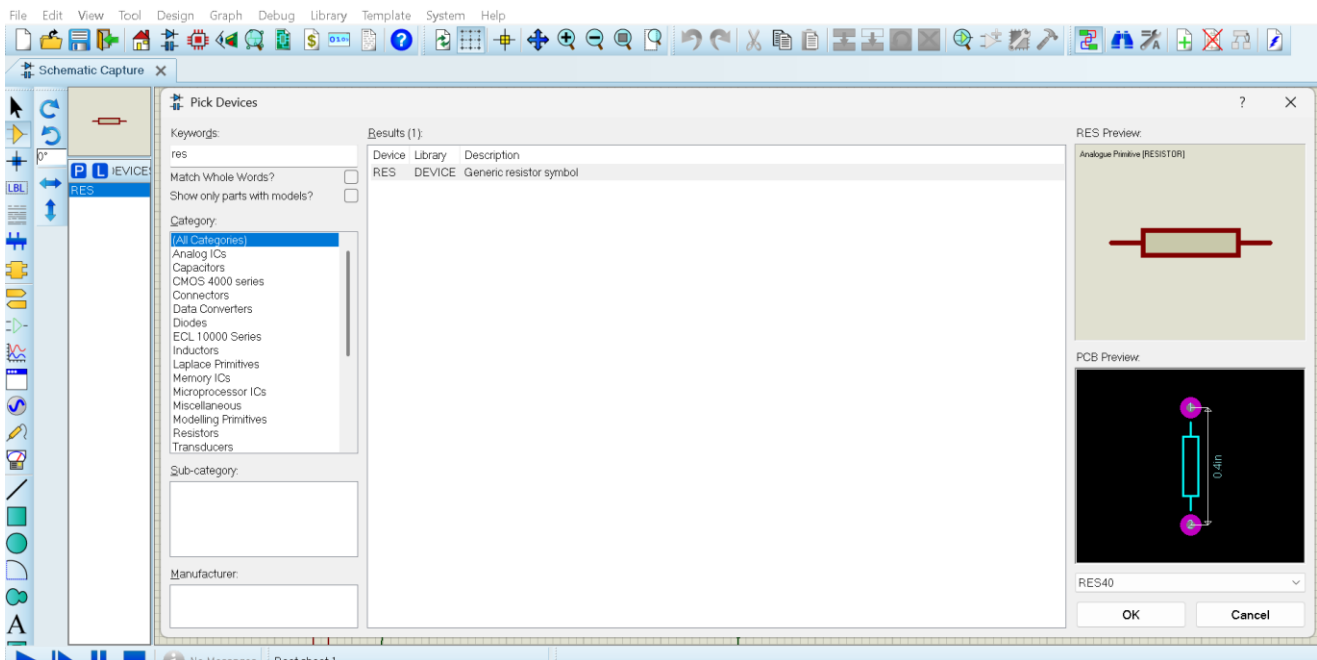


Steps I followed to create the circuit in Proteus

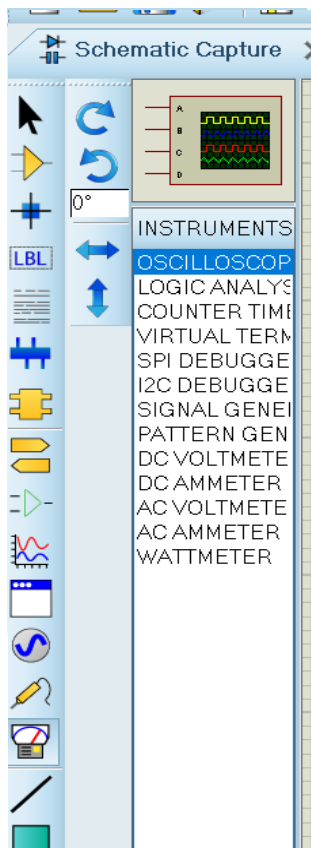
1. I opened the **Component Mode** tab, selected the **P** icon, searched for a **resistor**, and then placed it on the sheet.




2. After that, I opened the **Instrument** tab and placed the **signal generator** and **oscilloscope** onto the sheet.



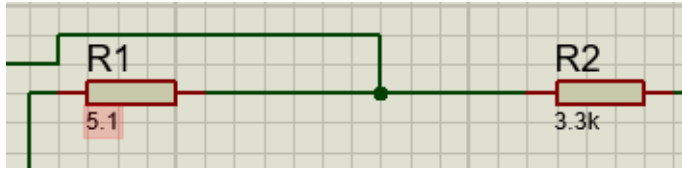
3. After that, I connected the two resistors in series by drawing a wire with the mouse, and then I set their resistance values to **R1 = 5.1 ohm** and **R2 = 3.3 ohm**.



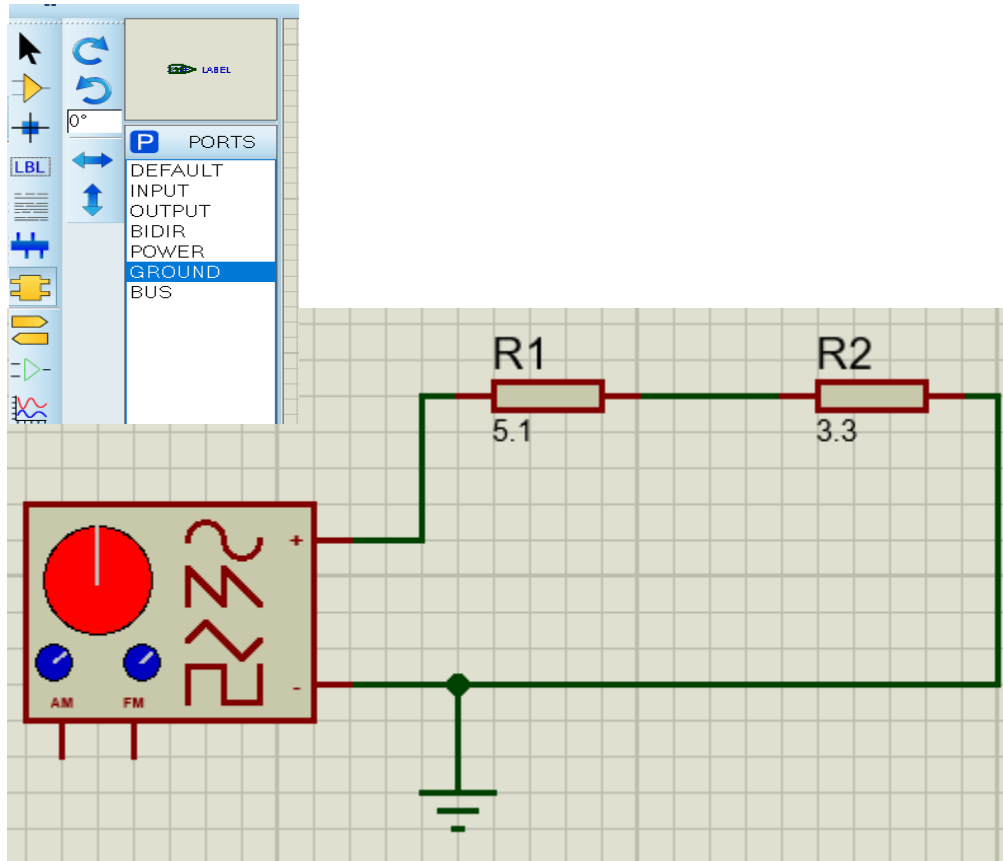4. After that, I connected the **positive terminal of the signal generator** to **R1**. The **negative terminal** was grounded by placing a **ground** from the **Subcircuit Mode**, and **R2** was also connected to the ground.



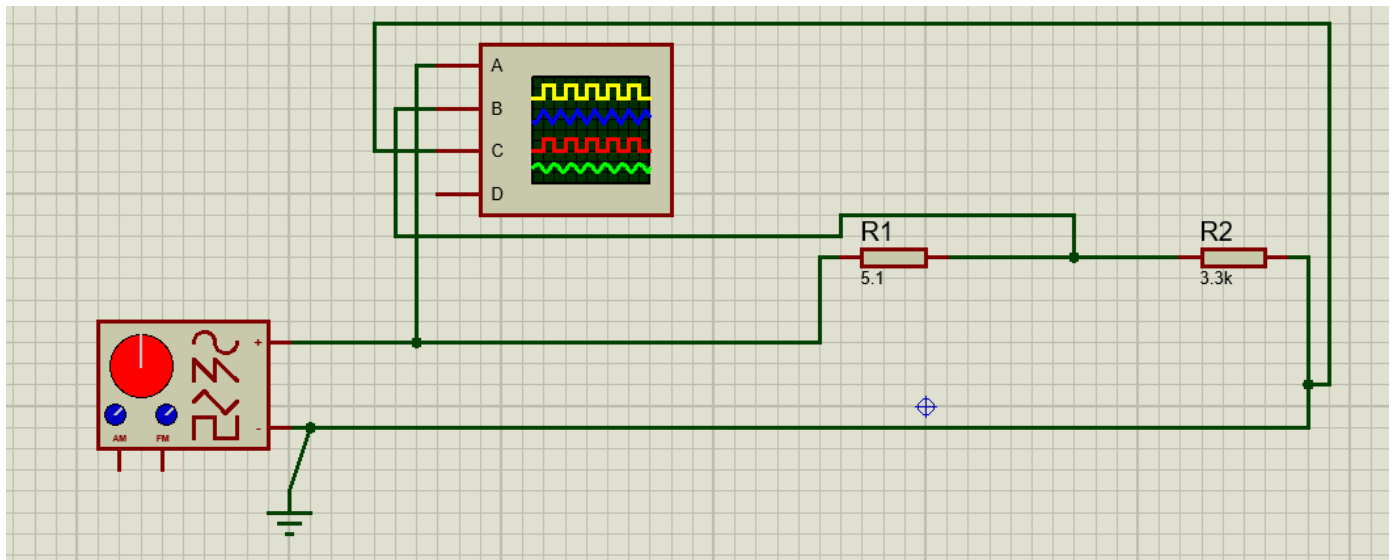5. Next, I connected **Channel A** of the oscilloscope between the **input** and **R1**, **Channel B** between **R1** and **R2**, and **Channel C** between **R2** and **ground**.



6. For the second experiment everything is same we just added another resistor in the series with R1, R2.

7. The Values of voltages and frequencies can be changed by just clicking on signal generator and modifying the properties.